

SEQUENCE GENERATOR

A sequence generator is a digital circuit that produces a predefined sequence of binary or numerical outputs. Sequence generators are commonly used in testing, encryption, communication systems, and state machines.

DESIGNING STEPS

- Find number of flip flops using $L \leq (2n - 1)$ where L is length of sequence, n indicate number of flip flop needed.
- Write truth table for this sequence using n flip-flops.
- Third step is the K-map optimization problem.

Binary Sequence Generator (1-0-1-1-0)

$L \leq (2n)$ here, $L=5$ hence, $n=4$

```
module sequence_generator_10110 (
    input clk,    // Clock signal
    input reset,  // Reset signal
    output reg seq_out // Sequence output
);
    // State encoding
    reg [2:0] state; // 3-bit state register to represent 5
    states

    // State Definitions
    parameter S0 = 3'b000, // State for '1'
        S1 = 3'b001, // State for '0'
        S2 = 3'b010, // State for '1'
        S3 = 3'b011, // State for '1'
        S4 = 3'b100; // State for '0'

    // Sequential Logic for State Transition
    always @(posedge clk or posedge reset) begin
        if (reset)
            state <= S0; // Reset to the initial state
        else begin
            case (state)
                S0: state <= S1; // 1 -> 0
                S1: state <= S2; // 0 -> 1
                S2: state <= S3; // 1 -> 1
                S3: state <= S4; // 1 -> 0
                S4: state <= S0;
                default: state <= S0; // Default to initial state
            endcase
        end
    end

    // Output Logic
    always @(*) begin
        case (state)
            S0: seq_out = 1;
            S1: seq_out = 0;
            S2: seq_out = 1;
            S3: seq_out = 1;
            S4: seq_out = 0;
            default: seq_out = 0;
        endcase
    end
endmodule
```

Fibonacci Sequence Generator

Generates a Fibonacci sequence

$$F_n = F_{n-1} + F_{n-2}$$

```
module fibonacci_generator (
    input clk,
    input rst,
    output reg [3:0] fib
);
    reg [3:0] prev1, prev2;
    always @(posedge clk or posedge rst)
        begin
            if (reset) begin
                prev1 <= 1; // Initialize first two no
                prev2 <= 0;
                fib <= 0;
            end else begin
                fib <= prev1 + prev2; // Fibonacci
                prev2 <= prev1;
                prev1 <= fib;
            end
        end
endmodule
```

Pseudo-Random seq

Uses Linear Feedback Shift Registers (LFSRs) to produce pseudo-random sequences.

```
module lfsr_sequence (
    input clk,
    input rst,
    output reg [3:0] lfsr
);
    always @(posedge clk or posedge rst)
        begin
            if (reset)
                lfsr <= 4'b1001;
            // Initialize LFSR with non-zero value
            else
                lfsr <= {lfsr[2:0], lfsr[3] ^ lfsr[2]};
            // Feedback for randomness
        end
endmodule
```

Gray Code Sequence

Produces a sequence where only one bit changes between consecutive states.

```
module gray_code_generator (
    input clk,
    input reset,
    output reg [2:0] gray
);
    reg [2:0] binary;
    always @(posedge clk or posedge
    reset) begin
        if (reset)
            binary <= 0;
        else
            binary <= binary + 1; // Increment in
        binary
    end
    always @(*) begin
        gray = binary ^ (binary >> 1); // Binary
        to Gray conversion
    end
endmodule
```

1. **Reset Behavior:** Ensure the generator starts with a known state.
2. **Timing and Clock:** Ensure timing constraints are met, especially in high-frequency applications.
3. **State Encoding:** Optimize the state representation for efficient hardware usage.
4. **Modularity:** Use parameters or constants to modify the sequence dynamically.




COUNTER

Synchronous Counter: synchronous counter has one global clock which drives each flip flop so output changes in parallel. $T_{\text{delay}} = t_{\text{pd}}$

Ring Counter

 Formed by connecting the output of last stage back to input of the shift register.



CLOCK FREQUENCY - $F/2N$

Drawback:

- Need to start the counter or need extra gate to make itself start.
- Can generate on N state


module ring_counter

```
(
  input wire clk,    // Clock input
  input wire reset,  // Active high reset
  output reg [3:0] q // 4-bit ring counter output
);
always @(posedge clk or posedge reset)
begin
  if (reset) begin
    q <= 4'b0001; // Initialize the ring counter
  end
  else begin
    q <= {q[2:0], q[3]}; // Rotate left
  end
end
endmodule
```

Johnson counter

Also called twisted ring counter/switched tail / Mobile walking

 Form by connecting complement of output of last stage back to input of shift register.



CLOCK FREQUENCY - $F/2N$


Drawback:

- High number of unused states.
- Enter to lock up state.

```
module johnson_counter(
  input wire clk,    // Clock input
  input wire reset,  // Active high reset
  output reg [3:0] q // 4-bit Johnson counter output
);
always @(posedge clk or posedge reset)
begin
  if (reset)
  begin
    q <= 4'b0000; // Initialize the counter
  end
  else
  begin
    q <= {q[2:0], ~q[3]}; // Shift left and invert the MSB
  end
end
endmodule
```

BCD COUNTER

```
module bcd_counter(
  input wire clk,    // Clock input
  input wire reset,  // Active high reset
  output reg [3:0] bcd // 4-bit BCD output
);
always @(posedge clk or posedge reset) begin
  if (reset) begin
    bcd <= 4'b0000; // Reset BCD counter to 0000
  end else if (bcd == 4'b1001) begin
    bcd <= 4'b0000; // Reset to 0000 when it reaches 9
  end else begin
    bcd <= bcd + 1;
  end
end
endmodule
```

 

DECODER COUNTER

```
module decade_counter(
  input wire clk,    // Clock input
  input wire reset,  // Active high reset
  output reg [3:0] count // 4-bit counter output
);
always @(posedge clk or posedge reset) begin
  if (reset) begin
    count <= 4'b0000; // Reset counter to 0000
  end else if (count == 4'b1001) begin
    count <= 4'b0000; // Reset to 0000 WHEN 9
  end else begin
    count <= count + 1; // Increment counter by 1
  end
end
endmodule
```

Asynchronous Counter: counter is a cascaded arrangement of flip-flops where the output of one flip-flop drives the clock input of the following flip-flop. $T_{\text{delay}} = t_{\text{pd}}$

Ripple counter

Clk	edge	nature
Q		DOWN
Q	●	UP
Q'	○	UP
Q'	●	DOWN


- All flip flop works in Toggle mode.
- Full state = $2n$, Full state = UP + DOWN
- For DOWN counter use PRESET and for UP counter use CLEAR
- ACTIVE HIGH- AND / OR & ACTIVE LOW- NAND / NOR
- DUTY TIME = (ON TIME) / (ON TIME + OFF TIME)

UP COUNTER

```

module up_counter(
    input wire clk,    // Clock input
    input wire reset,  // Active high reset
    output reg [2:0] count // 3-bit counter
);
    // Always block to handle counting on
    // positive clock edge or reset
    always @(posedge clk or posedge reset)
    begin
        if (reset)
            count <= 3'b000; // Reset counter 000
        else begin
            count <= count + 1; // Increment by 1
        end
    end
endmodule

```

 


DOWN COUNTER

```

module down_counter(
    input wire clk,    // Clock input
    input wire reset,  // Active high
    output reg [3:0] count // 4-bit counter
);
    // Always block to handle counting
    // on positive clock edge or reset
    always @(posedge clk or posedge
    reset)
    begin
        if (reset) begin
            count <= 4'b1111; // Reset to 1111
        end else begin
            count <= count - 1; // Decrement by 1
        end
    end
endmodule

```

 


UP/DOWN COUNTER

```

module up_down_counter(
    input wire clk,    // Clock input
    input wire rst,    // Active high
    input wire up_down, // Control
    output reg [3:0] count
);
    always @(posedge clk or posedge rst)
    begin
        if (reset) begin
            count <= 4'b0000; // Resst 0000
        end else
        if (up_down) begin
            count <= count + 1; // Increment (up)
        end else begin
            count <= count - 1; //Decrement(down)
        end
    end
endmodule

```

 

SYNCHRONOUS COUNTER

All flip flop are clocked at a time .

Faster, since all flip-flops change state simultaneously on the clock edge.

More complex due to the requirement for synchronizing all flip-flops.

Consumes more power, as all flip-flops are clocked simultaneously.

Errors are easier to control or detect due to synchronized state changes.

Suitable for high-speed, reliable counting applications like in CPUs or complex digital systems.

ASYNCHRONOUS COUNTER

Only the first flip-flop is driven by the clock. The other flip-flops are triggered by the output of the preceding flip-flop.

Slower, due to the propagation delay between flip-flops.

Simpler in design as only the first flip-flop is clocked.

Generally, consumes less power as only one flip-flop receives the clock signal.

Difficult to control or detect errors due to the asynchronous nature.

Suitable for simple, low-frequency counters or applications where speed is not critical.

