FIFO

FIRST IN FIRST OUT

A FIFO (First-In, First-Out) is a **queue-based memory buffer** where data is written into the queue in the order it arrives and is read in the same order. The principle follows a **first-come**, **first-served** approach, making it ideal for **buffering**, **data transfer**, **and synchronization** in digital systems.

FIFO Depth Calculation

The **depth** of a FIFO refers to the number of storage locations available for holding data before the buffer is full. It is crucial for ensuring proper data flow without overflow or underflow conditions.

The depth (D) of a FIFO can be calculated based on system parameters:

FIFO Depth Calculation

FIFO Depth ≥ (Max Data Rate In - Min Data Rate Out)×Latency+Margin

Where:

- Max_DataRate_In = Maximum input data rate
- Min_DataRate_Out = Minimum output data rate
- **Burst_Size** = Maximum burst size of incoming data

For single -clock FIFO:

If the FIFO is operating in a **single clock domain**, the depth is determined by the throughput requirements.

$$FIFODepth \geq \frac{MaxDataThroughput(words/sec) * Latency(sec)}{ClockPeriod(sec)}$$

For Asynchronous (Dual-Clock) FIFO

If the FIFO is crossing **two clock domains** (CDC), the depth is determined by the ratio of input and output clock frequencies:

$$FIFODepth \geq \frac{F_{write}}{F_{read}}*BurstSize + Margin$$

Where:

- **Fwrite** = Write clock frequency
- **Fread** = Read clock frequency
- **Burst Size** = Maximum burst of incoming data
- Margin = Safety margin (typically 10-20% of the calculated depth)

There are two types of FIFOs

- 1. Synchronous FIFO
- 2. Asynchronous FIFO

Synchronous FIFO

- Read and write operations occur under the same clock domain.
- Requires control logic for full, empty, and almost full/almost empty status.

FIFO Control Logic:

(a) FIFO Full Condition

A FIFO is **full** when the write pointer catches up to the read pointer after writing.

Full Condition: $(Wptr+1) \mod N = Rptr$

(b) FIFO Empty Condition

A FIFO is **empty** when the read pointer reaches the write pointer (i.e., no unread data is available).

Empty Condition: Wptr=Rptr

These flags are used to prevent **overflow** (writing to a full FIFO) or **underflow** (reading from an empty FIFO).

```
module synchronous_fifo
#(parameter DEPTH=8, DATA_WIDTH=8)
(input clk, rst_n,
 input w_en, r_en,
 input [DATA_WIDTH-1:0] data_in,
 output reg [DATA_WIDTH-1:0] data_out,
 output full, empty
 reg [$clog2(DEPTH)-1:0] w_ptr, r_ptr;
 reg [DATA_WIDTH-1:0] fifo[DEPTH];
// Set Default values on reset.
      always@(posedge clk) begin
       if(!rst_n) begin
       w_ptr \le 0; r_ptr \le 0;
       data out \leq 0;
       end
      end
// To write data to FIFO
 always@(posedge clk) begin
  if(w_en & !full)begin
   fifo[w_ptr] <= data_in;
   w_ptr \le w_ptr + 1;
  end
 end
// To read data from FIFO
 always@(posedge clk) begin
  if(r_en & !empty) begin
   data_out <= fifo[r_ptr];</pre>
   r_ptr \le r_ptr + 1;
```

assign full = ((w ptr+1'b1) == r ptr);

assign empty = (w_ptr == r_ptr);

end end


endmodule

Depth of FIFO: The number of slots or rows in FIFO is called the depth of the FIFO.

Width of FIFO: The number of bits that can be stored in each slot or row is called the width of the FIFO.

Working Principle

 - Data is written into the FIFO on a same clock edge till FIFO full.
- Data is read from the FIFO on a same clock edge till FIFO empty.



Advantages of Synchronous FIFO

- :: Simple control logic due to a single clock domain.
- :: Faster and more power-efficient compared to asynchronous FIFOs.
- :: Easier to implement in hardware (FPGAs, ASICs) using Block(BRAM).
- :: Low latency and high-speed data transfer.

Applications of Synchronous FIFO

- Data buffering in processors and communication interfaces
- Pipeline processing in DSP (Digital Signal Processing)
- Networking devices for buffering
- Audio and video streaming systems
- Memory controllers for temporary data storage

Asynchronous FIFO

An Asynchronous FIFO is a type of FIFO memory used to transfer data between two different clock domains. It allows smooth data communication between two circuits that operate on different clock frequencies.

- >> Many digital systems have **different clock domains** for different components.
- >> A direct connection between these domains causes metastability issues.
- >> Asynchronous FIFOs ensure reliable data transfer between these domains without data loss or corruption.

Pointer Synchronization Using Gray Code

- Directly passing binary pointers between different clock domains causes **metastability issues**.
- Solution: Convert binary pointers to Gray code before passing them to the other clock domain.

Gray code ensures that only **one-bit changes at a time**, reducing errors.

VERILOG CODE

endmodule

```
//FIFO full condition
wfull = (g_wptr_next ==
{~g_rptr_sync[PTR_WIDTH:PTR_WIDTH-1],
```

//FIFO empty conditionFIFO

```
rempty = (g_wptr_sync == g_rptr_next);
```

```
///FIFO WRITE POINTER HANDLER
module wptr_handler #(parameter PTR_WIDTH=3) (
 input wclk, wrst_n, w_en,
 input [PTR_WIDTH:0] g_rptr_sync,
 output reg [PTR_WIDTH:0] b_wptr, g_wptr,
 output reg full
reg [PTR_WIDTH:0] b_wptr_next;
  reg [PTR_WIDTH:0] g_wptr_next;
  reg wrap_around;
  wire wfull;
 assign b_wptr_next = b_wptr+(w_en & !full);
 assign g wptr next = (b wptr next >>1)^b wptr next;
 always@(posedge wclk or negedge wrst_n) begin
    if(!wrst n) begin
      b_wptr <= 0; // set default value
      g_{wptr} \le 0; end
     else begin
      b_wptr <= b_wptr_next; // incr binary write pointer</pre>
      g_wptr <= g_wptr_next; // incr gray write pointer
     end
  end
 always@(posedge wclk or negedge wrst_n) begin
  if(!wrst_n)
    full \ll 0;
  else
    full <= wfull;
 end
assign wfull =
(g_wptr_next=={~g_rptr_sync[PTR_WIDTH:PTR_WIDTH-1],
g_rptr_sync[PTR_WIDTH-2:0]});
```


//FIFO READ POINTER

```
module rptr_handler #(parameter PTR_WIDTH=3) (
 input rclk, rrst_n, r_en,
 input [PTR_WIDTH:0] g_wptr_sync,
 output reg [PTR_WIDTH:0] b_rptr, g_rptr,
 output reg empty
); reg [PTR_WIDTH:0] b_rptr_next;
 reg [PTR_WIDTH:0] g_rptr_next;
assign b_rptr_next = b_rptr+(r_en & !empty);
assign g_rptr_next = (b_rptr_next >>1)^b_rptr_next;
assign rempty = (g_wptr_sync == g_rptr_next);
always@(posedge rclk or negedge rrst_n) begin
  if(!rrst_n) begin
   b_rptr \le 0;
   g_rptr \le 0;
  end else begin
   b_rptr <= b_rptr_next;
   g_rptr <= g_rptr_next;</pre>
  end
 end
 always@(posedge rclk or negedge rrst_n) begin
  if(!rrst_n) empty <= 1;
  else
           empty <= rempty;
 end
endmodule
```

///FIFO MEMORY

endmodule

```
module fifo_mem #(parameter DEPTH=8,
DATA_WIDTH=8, PTR_WIDTH=3) (
input wclk, w_en, rclk, r_en,
input [PTR_WIDTH:0] b_wptr, b_rptr,
input [DATA_WIDTH-1:0] data_in,
input full, empty,
output reg [DATA_WIDTH-1:0] data_out);
reg [DATA_WIDTH-1:0] fifo[0:DEPTH-1];
always@(posedge wclk) begin
if(w_en & !full) begin
fifo[b_wptr[PTR_WIDTH-1:0]] <= data_in;
end end
assign data_out = fifo[b_rptr[PTR_WIDTH-1:0]];
```

 

//TOP MODULE

```
`include "synchronizer.v"
`include "wptr_handler.v"
`include "rptr_handler.v"
`include "fifo mem.v"
module asynchronous_fifo #(parameter DEPTH=8, DATA_WIDTH=8) (
 input wclk, wrst_n,
 input rclk, rrst_n,
 input w_en, r_en,
 input [DATA_WIDTH-1:0] data_in,
 output reg [DATA_WIDTH-1:0] data_out,
 output reg full, empty
 parameter PTR_WIDTH = $clog2(DEPTH);
 reg [PTR_WIDTH:0] g_wptr_sync, g_rptr_sync;
 reg [PTR_WIDTH:0] b_wptr, b_rptr;
 reg [PTR_WIDTH:0] g_wptr, g_rptr;
 wire [PTR_WIDTH-1:0] waddr, raddr;
synchronizer #(PTR_WIDTH) sync_wptr (rclk, rrst_n,g_wptr,g_wptr_sync);
//write pointer to read clock domain
synchronizer #(PTR_WIDTH) sync_rptr (wclk, wrst_n, g_rptr, g_rptr_sync);
//read pointer to write clock domain
```

fifo_mem fifom(wclk, w_en, rclk, r_en,b_wptr, b_rptr, data_in,full,empty,

wptr_handler #(PTR_WIDTH) wptr_h(wclk, wrst_n,

rptr_handler #(PTR_WIDTH) rptr_h(rclk, rrst_n,

w_en,g_rptr_sync,b_wptr,g_wptr,full);

r_en,g_wptr_sync,b_rptr,g_rptr,empty);

data_out);

endmodule

d_out <= 0; end else begin q1 <= d_in; d_out <= q1; end</pre>

//2 FLIP-FLOP SYNCHRONIZER

d_out);

end endmodule

reg [WIDTH:0] q1;

if(!rst_n) begin q1 <= 0;

always@(posedge clk) begin

module synchronizer #(parameter WIDTH=3) (input clk, rst_n, [WIDTH:0] d_in, output reg [WIDTH:0]

Applications of Asynchronous FIFO

- Clock Domain Crossing (CDC)
- Processor to Peripheral Communication
- High-speed data Acquisition Systems
- Network Routers & Switches (Packet Buffers)
- Audio & Video Processing Systems
- FPGA-Based Designs (Bridging Different IP Blocks)
- USB & PCIe Communication
- Software-Defined Radio (SDR) & Wireless Communication
- Video Frame Buffers in GPUs